

# Index

---

- 1080i - 838 -  
12AT7 (ECC81) - 214 -  
12AU7 (ECC82) - 215 -  
12AX7 (ECC83) - 215 -  
300B (valve) - 223 -  
5.1 multi-channel audio - 624 -  
6072 (valve) - 217 -  
6L6, 6V6, 807 and KT66 Dynasty - 218 -  
720p/60 and 720p/59.94 - 840 -  
845 (valve) - 226 -  
Absorption - 82 -  
AC circuits - 14 -  
AC100 amplifier - 758 -  
AC701 valve - 218 -  
Acoustic (Double) bass - 135 -  
Acoustic guitar and classical guitar - 129 -  
Acoustic treatment - 89 -  
Acoustical analysis of loudspeaker in an infinite baffle - 783 -  
Acoustical power required for realistic listening levels - 62 -  
Active Crossovers - 795 -  
Active devices - 153 -  
Additive synthesis - 435 -  
ADT (or Flanging) - 482 -  
AES/EBU or IEC958 Type 1 Interface - 527 -  
AIFF & AIFC - 545 -  
AKG 414 - 123 -  
AKG Model C 12- 122 -  
Aliasing - 487 -  
All-pass filters, phase-rotators and the Symmetra-Peak - 407 -  
Altec Duplex loudspeakers - 810 -  
Altec Lansing 436C - 397 -  
Alternatives to inductors - 369 -  
Ambisonics - 630 -  
Amplification - 176 -  
Amplifier as part of the sound - 739 -  
Amplifier myths exploded - 767 -  
Amplifiers for High Quality Monitoring - 701 -  
Analogue Mastering - 480 -  
Analogue Multi-track Tape Machines - 481 -  
Analogue Noise Generators - 426 -  
Analogue Sequencers - 443 -  
Analogue video interfaces - 832 -  
Analysis of equivalent circuits - 787 -  
Angular frequency - 19 -  
Aperture effect - 488 -  
Applications of digital tape recorders - 536 -  
Aristotle just got wired! - 500 -  
Artificial echo - 375 -  
Artificial reverberation - the echo chamber - 374 -  
Artzt circuit (a.k.a. the SRPP and the  $\mu$ -follower) - 205 -  
Aspect ratio - 841 -  
Asynchronous sample-rate conversion - 597 -  
Attack – Decay - Sustain - Release (ADSR) Generator - 425 -  
Attenuation networks and early microphone mixers - 670 -  
AU Files - 546 -  
Audio and the PC - 571 -  
Audio Data Files - 544 -  
Audio editor - 302 -  
Audio Enhancers - 408 -  
Audio Mixer Circuitry - 658 -  
Audio Scenes - 593 -  
Audio Watermarking - 596 -  
Axial (first-order) eigentones for a small room - 85 -  
B&W 801 monitoring loudspeaker - 815 -  
BA284 preamplifier - 691 -  
Baby Boom - 625 -  
Bailey's Transmission-Line loudspeaker - 792 -  
Bass drum - 132 -  
Bass-boost circuit - 365 -  
Bass-cut circuit - 362 -  
Bass-Reflex enclosure - 786 -  
Baxandall tone-control circuit - 367 -  
BBC LS3/5(a) - 812 -  
BBC LS5/8 - 813 -  
BBC LS5/9 - 815 -  
BBC Radiophonic Workshop - 415 -  
Bench power supply - 300 -  
Bessel - 181 -  
Beware exploding capacitors - 287 -  
Beware the guitar-amplifier mains-transformer - 287 -  
Beyond 255 and below zero - 510 -  
Bias - 474 -  
Binary arithmetic - 507 -  
Binaural Techniques - 600 -  
Bipolar junction transistors (BJTs) - 246 -  
Bits and bytes - 508 -  
Blumlein  $\delta$  (or difference) technique or TIHM - 148 -  
Blumlein's (intensity derived) system - 602 -  
Brass - Trumpet and Trombone - 137 -  
Bridge configuration - 731 -  
Building acoustics - 82 -  
Building complex waveforms from sine waves - 41 -  
Bungee-jumping into differential equations - 161 -  
Butterworth - 182 -  
BWF - 545 -  
Capacitances in series and parallel - 24 -

# Index

---

- Capacitor ESR - 305 -  
Capacitor - 17, 95, 303 -  
Cardioid microphones - 100 -  
Cascode circuit - 204 -  
Cathode and the work function - 209 -  
Cathode follower - 200 -  
Cathode Ray Oscilloscope (CRO) - 293 -  
Cathode ray tube and raster scanning - 824 -  
Cathode stripping and the "standby" switch - 768 -  
Cathode-bias or fixed-bias - 710 -  
CD player as a signal generator - 298 -  
CD Rainbow - 548 -  
Celestion G12, and the "Blue" - 809 -  
Cello - 134 -  
Channel Modes - 449 -  
Characteristic Curves - 191 -  
Chassis material - 773 -  
Chebyshev - 180 -  
Choice of components - 770 -  
Circuit simulation - the virtual electronics laboratory - 301 -  
Circuits with memory - 505 -  
Class AB - 700 -  
Class-A - 699 -  
Class-B - 699 -  
Class-D amplifiers - 732 -  
Class-D, Class-G and Current Dumping - 700 -  
Class-G amplifiers - 731 -  
Classic amplifiers- 745 -  
Classic consoles - 669 -  
Classic guitar amplifier loudspeaker drivers - 808 -  
Classic microphones - 107 -  
Classic moving-coil monitoring loudspeakers - 810 -  
Clicks, Streamers and Punches - 858 -  
Clock Signal - 836 -  
CMOS - 503 -  
Coincident (X-Y) technique - 141 -  
Colour Perception - 827 -  
Colour Television - 828 -  
Colours of Noise - 426 -  
Combined controls (tone) - 366 -  
Commercially available valves - 210 -  
Common-cathode amplifier - 196 -  
Common-grid (or earthed-grid) amplifier - 199 -  
Compact Cassette- 478 -  
Compact Disc - 547 -  
Complementary functions - 163 -  
Complete audio test-sets - 299 -  
Complex FM and feedback - 431 -  
Complex numbers - 20 -  
Components, units and multipliers - 7 -  
Compounds and bonds - 3 -  
Compressed file formats - 546 -  
Conductors and insulators - 5 -  
Connectors - 318 -  
Consonance and dissonance - 52 -  
Controllers - 448 -  
Convolution - 556 -  
Convolutional reverberation - 380 -  
Counters - 511 -  
Creating the stereo picture - panning - 139 -  
Creative Uses of Tape - 482 -  
Crest factor - 62 -  
Critical band - 74 -  
Crossed cardioids- 144 -  
Crossed eights or crossed cosine-microphones - 142 -  
Crossover Networks - 794 -  
Crosstalk-cancellation - 601 -  
Current and voltage generators - 13 -  
Current Dumping - The Quad 405 - 722 -  
Current sources and current mirrors - 258 -  
CV and Gate Control - 443 -  
Darlington Pair - 254 -  
Data Compression Techniques - 584 -  
Data Format - 531 -  
Data rates and Picture formats - 550 -  
Data rates - 541 -  
Data - 528 -  
DC Coupling - 717 -  
DC Offset Protection - 718 -  
Decca Tree - 147 -  
Decibel - 59 -  
De-Essers - 409 -  
Delay-derived stereophony - the Precedence effect or Law of the first wave-front - 608 -  
Delay-Locked Loop (and the Phase-Locked Loop) - 522 -  
Derivation of band-pass and high-pass filters - 559 -  
Design of auditoria - 83 -  
Designing an FIR filter - 560 -  
Designing an IIR filter - 561 -  
Designing digital filters - 560 -  
Development of Pentode and Beam Tetrode - 193 -  
Differential equations - 160 -  
Diffusion - 83 -  
Digital amplifiers - 735 -  
Digital audio analyser - 300 -  
Digital audio recording - 534 -  
Digital Audio Stationary Head (DASH) Format - 536 -  
Digital Audio Stationary Head (DASH) multitrack format - 537 -  
Digital audio tape recorders - 534 -  
Digital consoles - 668 -  
Digital electronics - 497 -

# Index

---

- Digital filtering - 555 -  
Digital filters - 184 -  
Digital Fourier Transform - 40 -  
Digital Line-up - 649 -  
Digital Manipulation - 669 -  
Digital Mastering - 536 -  
Digital Mixer Architecture - 669 -  
Digital Multi-tracks - 537 -  
Digital reverberation - 379 -  
Digital Rights Management (DRM) and  
MPEG-21 - 595 -  
Digital to analogue conversion - 488 -  
Digital Visual Interface (DVI) and HDMI  
- 849 -  
Digital waveform generation - 338 -  
Digital-machine based representation of  
numbers - 507 -  
Diode as a rectifier - 189 -  
Diode as detector - 187 -  
Diode - 226 -  
Direct injection and hum loops - 655 -  
Disc Drive Technology - 539 -  
Discrete Fourier Transform - 491 -  
Discrete op-amps - 272 -  
Distortion in passive components - 309 -  
Distortion meter and wave analyser - 298 -  
Dither - 489 -  
DIY "Boutique" amplification - towards a  
personal aesthetic - 769 -  
DMA - 519 -  
Dolby AC-3 - 590 -  
Dolby B - 479 -  
Dolby Digital Surround EX - 629 -  
Dolby E - 591 -  
Dolby Surround and Pro-Logic - 628 -  
Doping - 239 -  
Double Tracking - 482 -  
Double-triodes - 212 -  
DRAM - 520 -  
Droop - power-supply issues in instrument  
amplifiers - 767 -  
Drum kit - 131 -  
DSP and Amplification - 778 -  
DSP effect and instrument Plug-ins - 576 -  
DTS - 592 -  
Dual-diaphragm capacitor microphones  
- 104 -  
Dumble and Trainwreck amplifiers - 765 -  
Dust and scratches - 464 -  
DVD Recordable (DVD-R) - 552 -  
DVD - 549 -  
DVD-A - 553 -  
Dynamic range - 315 -  
Dynamics Processors - 392 -  
Early electronic music - 412 -  
Early experiments - 321 -  
Echo and Reverberation - 374 -  
Echo hiding - 596 -  
Echo send and return - 679 -  
Eckmiller equalisation - 685 -  
ECL and LVDS - 504 -  
Edison effect - 185 -  
Effect of age upon hearing sensitivity  
- 80 -  
Effect on frequency response and  
distortion - 266 -  
Effect Send and Return - 662 -  
EL34 - 222 -  
Electret - 97 -  
Electric field, potential difference and  
electric current - 5 -  
Electric guitar and bass guitar - 130 -  
Electric Guitar - 341 -  
Electric pianos - 356 -  
Electric shock - 285 -  
Electrical Format - 532 -  
Electrical, mechanical and acoustical  
analogies - 31 -  
Electricity discovered - 5 -  
Electricity - 1 -  
Electric-Road amplifier - 770 -  
Electrodynamic microphones - 94 -  
Electromagnetic waves - 28 -  
Electron paths - 190 -  
Electronic organs - 331 -  
Electronics construction - 287 -  
Electrons inside the valve - 186 -  
Electrons - 3 -  
Electrostatic Loudspeakers - 805 -  
Electrostatic microphones - 95 -  
Elektronische Musik - the German School  
- 412 -  
Elusive VF14 - 117 -  
Embedded audio in HDTV - 843 -  
Embedded clocks - 515 -  
Embedded Digital Audio in the Digital  
Video Interface - 842 -  
EMF - 6 -  
EMI levels - 679 -  
EMI RS124 - 398 -  
Emitter Follower - 253 -  
Encode - decode - 605 -  
Energy - 9 -  
Envelope Generation and the VCA - 423 -  
Equalisation (tone control) - 92, 360, 464,  
475 -  
Equalisers and tone-controls - 660 -  
Equalisers - 657 -  
Equivalent circuit for the transistor - 250 -  
Equivalent circuit of a pentode - 196 -  
Equivalent circuit of a valve - 196 -  
Equivalent circuits - 153 -  
Evolution - 519 -  
Exotic op-amps - 272 -  
Expansion – Noise reduction - 405 -  
Eye pattern - 524 -

# Index

---

- Faders and Pan Controls - 662 -  
Faders - 670 -  
Fairchild 660 and 670 - 399 -  
Fairlight CMI II and the Synclavier - 433 -  
Falling wavelengths - 463 -  
Faster rates of attenuation - 365 -  
Feed-forward and Feedback Compressors - 396 -  
Fender "Champ" (5C1) - 749 -  
Fender "Deluxe" (5D3) - 750 -  
FET Compressor - UREI 1176 - 400 -  
Fibre Channel - 542 -  
Fibre-optic format - 532 -  
Field Programmable Gate Arrays - 521 -  
Field-Effect Transistor (FET) - 254 -  
Filter design - 180 -  
Filter Templates - 836 -  
Finite baffle - 790 -  
FIR and IIR digital filters - 557 -  
FireWire Interface - 543 -  
FLAC - 546 -  
FLAC - 592 -  
Flanging, Phasing and Chorus - 388 -  
Flash memory - 521 -  
Fletcher-Munson Curves (equal loudness contours) - 73 -  
FM Sound Synthesis - 428 -  
FM Theory - 428 -  
Fourier once again.... - 846 -  
Fourier Transform - 35 -  
Fourier - 34 -  
Fourier's Uncertainty Principle - 497 -  
Frame by frame - 844 -  
FRANCINSTIEN viewed as a head-shadow compensator - 621 -  
French Horn(s) - 136 -  
Frequency response - 344 -  
Frequency response - 42 -  
Frequency response - 559 -  
Frequency response - 97 -  
From generators to music - 13 -  
From uA702 to uA741 - 268 -  
Full Frame - 856 -  
Functional physical modelling - 437 -  
Fuzz - 383 -  
Genelec 8050A - 817 -  
Generators - 12 -  
Getter - 210 -  
Gibson GH-40 - 759 -  
Good workshop practice - 286 -  
GOP - 845 -  
Gramophone records (78s and LPs) - 460 -  
Granular synthesis - 438 -  
Green Book, White Book and Blue Book - 549 -  
Group-delay perception - 78 -  
Groups Revisited - 653 -  
Groups - 651 -  
H sync and V sync - 825 -  
Hafler circuit - 623 -  
Hammond organ - 350 -  
Hard Disc Recording - 538 -  
Hard Drive Interface Standards - 541 -  
Hard-Disc Editing - 571 -  
Harmonic Series - 54 -  
Harmonics - 55 -  
HDMI (High-Definition Multimedia Interface) - 850 -  
HDTV Standards - 838 -  
Headphones - 819 -  
Heater DC supply - the Schottky diode - 773 -  
Helios - 694 -  
Hexadecimal base - 507 -  
HF crosstalk compensation - 617 -  
HF imaging - 605 -  
High Definition Television (HDTV) - 837 -  
Higher order transfer functions - 176 -  
High-pass example - 564 -  
High-voltage audio distribution systems and long-line PA - 738 -  
Hi-hat - 133 -  
History - 485 -  
History - 743 -  
Hohner Clavinet - 356 -  
Hole current - 241 -  
Horn Loudspeakers - 800 -  
How to avoid differential equations - or Fourier's big cheat - 169 -  
Hyper-Threading or Multi-Threading - 519 -  
IDE Drives - 541 -  
IIR filter design example - 562 -  
Impedance and efficiency - 820 -  
Impedance transformation - 16 -  
Improving Image Sharpness by means of Inter-channel Crosstalk - 616 -  
Improving stereo - 616 -  
Impulse response - 557 -  
Inductor-gyrators - 661 -  
Inductors in series and parallel - 24 -  
Inductors - 19 -  
Infinite baffle - 782 -  
Input and Output Impedance - 154 -  
Input Strip - 650 -  
Insert points and Sends and Returns - 653 -  
Insert Points - 659 -  
Integrated power amplifiers - 729 -  
Intensity stereo coding - 589 -  
Interaction between amplifier and loudspeaker - 742 -  
Interfaces - 527 -  
Intermediate Compression Systems - 586 -  
Intermodulation distortion - 159 -

# Index

---

- Introduction to Digital Signal Processing (DSP) - 555 -  
Invention of the Triode - 189 -  
Inverse square law - 64 -  
Ionic and covalent bonds - 3 -  
Is it true that "nothing is transparent"? - 313 -  
Is there any validity in these ideas? - 311 -  
ITU-R Rec. 601 Description - General - 833 -  
Jensen P10R (the Bassman Loudspeaker) - 808 -  
John Linsley Hood's 10 watt, class-A amplifier - 718 -  
JTM100 - 751 -  
Junction FET (JFET) - 255 -  
Karlheinz Stockhausen - 413 -  
Kirchhoff's Laws - 7 -  
KT88 - 221 -  
Laplace Transform - 178 -  
Latency - 579 -  
LC circuits and resonance - 22 -  
Leakage and Windowing - 492 -  
Least Significant Bit (LSB) Modification - 596 -  
Leslie Loudspeaker - 818 -  
Limitations in digital signal processing - 568 -  
Line Level Stages - 665 -  
Linear systems - 154 -  
Line-array of loudspeakers- 804 -  
Listening tests - 313 -  
Listening tests, or do you have golden ears? - 310 -  
Logic analysers - 296 -  
Logic families - 502 -  
Logic gates and functions - 497 -  
Longitudinal Timecode (LTC) - 853 -  
Long-tailed pair - 202 -  
Long-tailed pair - 259 -  
Loss of the Shuffler - 607 -  
Lossless Compression - 585 -  
Loudspeaker equalisation - 798 -  
Loudspeakers in pipes - 788 -  
Louis and Bebe Barron - 414 -  
Low frequency directional hearing - 602 -  
Low Frequency Oscillator (LFO) - 425 -  
Low Level Tones - 596 -  
Low Voltage Technologies - 505 -  
Low-noise design- 262 -  
Low-noise pentodes - 211 -  
LR circuits - 364 -  
M4P - 546 -  
MADI - Serial Multi-channel Audio  
Digital Interface - 531 -  
Magnetic recording - 472 -  
Magnetic Theory - 473 -  
Magnetism and Electricity - the Dynamic Duo - 11 -  
Magnitude of the transfer function - 172 -  
Major fifth - 56 -  
Major third - 56 -  
Manufacture - 471 -  
Marconi Type A - 109 -  
Marshall - JTM45 - 750 -  
Masking - 74 -  
Mastering on the PC - 582 -  
Mastering, duplication and replication - 581 -  
Matchless and the boutique amplifier movement - 760 -  
Mathematical models for valves - 226 -  
Matter - 1 -  
Measurement of reverberation - 86 -  
Measurement of Sound Pressure Level (Sound Intensity Level) - 61 -  
Measuring sound - 59 -  
Mechanical analogies and the Theile-Small Parameters - 788 -  
Mechanical limitations - 462 -  
Mechanism of sampling - 486 -  
Mel - 62 -  
Mellotron - the electromagnetic sampler - 358 -  
Metal bonds - 4 -  
Metalwork and woodwork - 290 -  
Metamerism - the great colour swindle - 828 -  
Microcomputers and microprocessors - 516 -  
Microphone dynamic range - 105 -  
Microphone mixers - 671 -  
Microphone pre-amplifiers - 658 -  
Microphone technique for 5.1 audio - 626 -  
MIDI messages - 452 -  
MIDI Sequencing- 450 -  
MIDI Specification - 445 -  
MIDI System-Exclusive Messages - 450 -  
MIDI Timecode - 449 -  
MIDI Timecode, MIDI clocks and Song Position Pointers (SPPs) - 855 -  
MIDI - 444 -  
MIDI - 47 -  
Minor seventh chords and the dominant seventh - 57 -  
Mix amplifiers - 662 -  
Mixer Automation - 667 -  
Modern "classics" - 126 -  
Modern microphone circuitry - 127 -  
Modern techniques - 778 -  
Modern trends in synthesiser design - 435 -  
Modular synthesisers - 419 -  
Modulation spectra - 188 -

# Index

---

- Modulation - 58 -  
Moog and Carlos and the birth of commercial synthesisers - 418 -  
Moog MINIMOOG - 427 -  
More about MPEG-4 Part 3 (ISO/IEC 14496-3) - 593 -  
MOSFET - 256 -  
MOSFETs - 728 -  
Motional feedback - 799 -  
Moving coil - 94 -  
Moving-coil loudspeaker - 781 -  
MP3 - 546 -  
MP4 and M4A - 546 -  
MPEG layer 1 compression (PASC) - 587 -  
MPEG Layer 2 audio coding (MUSICAM) - 589 -  
MPEG Layer 3 - 589 -  
MPEG-4 Audio Lossless Coding (MPEG-4 ALS) - 546 -  
MPEG-4 Part 3 ISO/IEC 14496-3  
Advanced Audio Coding (AAC) - 590 -  
Multi-meter - 291 -  
Multiplexers - 502 -  
Multiplication - 509 -  
Multi-track Hard-Disc recording - 575 -  
Multivibrator - 335 -  
Music and acoustics - 44 -  
Music recognition by machine - 583 -  
Music Spotting Notes - 858 -  
Music theory - 46 -  
Musical notation - 48 -  
Musical Ranges - 46 -  
Musical Scales and Temperaments - 51 -  
Mute switch - 768 -  
MXL R144 Ribbon Microphone - 128 -  
Natural frequency - 167 -  
Near and Far Field - 66 -  
Negative feedback - 264 -  
Neumann M49 and M50 - 120 -  
Neumann U47 and U48 microphones - 115 -  
Neve 1073 - 689 -  
New techniques in pitch shifting and time-stretching - 569 -  
Ninths, elevenths and thirteenths - 57 -  
Noise exposure and hearing loss - 81 -  
Noise in a junction FET (JFET) - 264 -  
Noise - 106 -  
Noise, dynamic range and signal-to-noise - 177 -  
Non-linearity and harmonic distortion - 156 -  
Non-sinusoidal oscillators or waveform generators - 334 -  
Note names - 48 -  
Note-on and Note-off - 447 -  
NTSC and PAL or "composite" colour systems - 829 -  
Numerical coding of digital audio signals - 490 -  
OGG - 546 -  
Ohm's law - 7 -  
Olson-Belar RCA sound synthesiser - 417 -  
OM 3D Sound Processor - 635 -  
OM panning circuits - 636 -  
Ondes Martinot - 327 -  
Op-Amp Cookery - 275 -  
Op-amps - 266 -  
Operating system - 520 -  
Optical techniques - 403 -  
Opto-electronic Level Indication - 646 -  
Orange Book - 549 -  
Origin of the elements - 2 -  
ORTF technique - 147 -  
Output Transformers - 703 -  
Output-Stage Protection - 717 -  
Overheads - 133 -  
Overload point - 106 -  
PAL and NTSC - 854 -  
Pan Control - 652 -  
Parallel and serial presentations of digital data - the shift-register - 514 -  
Parallel digital interface - 837 -  
Parallel output devices - 730 -  
Particular integral- 168 -  
Patching - 426 -  
Peak-current - 246 -  
Pentatonic and Blues scale - 54 -  
Pentode acting as a triode - 230 -  
Pentode and beam-tetrode - 228 -  
Perceived fundamental - 430 -  
Perception of phase - 76 -  
Persistence of Vision - 823 -  
Phantom power - 659 -  
Phase distortion and electrostatic loudspeakers - 807 -  
Phase of the transfer function - 173 -  
Phase-shift oscillator - 334 -  
Phon - 61 -  
Photo-electric instruments - 323 -  
Phrase Sampling - 580 -  
Physical modelling - 436 -  
Physics of Magnetic Tape - 473 -  
Physics of Sound - 33 -  
Physiology of Hearing - 69 -  
Pianoforte - 131 -  
Pickup placement - 344 -  
Pick-up selection and tone controls - 347 -  
Pickup sensitivities and recorded velocities - 467 -  
Pitch Shifting - 386 -  
Pitch-correction - 390 -  
Plate reverb - 378 -  
PN junctions - 239 -

# Index

---

- Polar diagrams - 98 -  
Polar displays - 648 -  
Potential divider - 10 -  
Power Supply Regulator - 721 -  
Power Transistors - 276 -  
Power valves - 218 -  
Power - 9 -  
PPM and VU ballistics - 646 -  
PPM Meter - 644 -  
Practical capacitor microphones - 103 -  
Practical Components - 303 -  
Practical design - 249 -  
Practical Digital Audio Interface - 530 -  
Practical high-gain amplifiers - 261 -  
Practical instruments - 336 -  
Practical operational amplifiers in audio  
- 267 -  
Practical semiconductor designs - 718 -  
Practical sound absorbers - 90 -  
Practical transformers - 16 -  
Practical Valve Circuits - 194 -  
Preferred values for resistors - 309 -  
Pressure amplitude and SPL - 60 -  
Pressure Gradient or Velocity  
microphones - 99 -  
Pressure Microphones - 98 -  
Pressure or velocity - 98 -  
Pressure Zone Microphone (PZM) - 104 -  
Principles - 93 -  
Problems with Ambisonics - 632 -  
Professional analogue-audio levels - 320 -  
Proximity effect or bass tip-up - 102 -  
Psychoacoustic Masking Systems - 586 -  
Psychology of Hearing - 71 -  
Public address - 736 -  
Pultec EQP-1A - 370 -  
Q - 661 -  
Quad 303 circuit - 720 -  
Quantisation throttle - 847 -  
Quantisation - 487 -  
Quarter Frame message - 855 -  
Rack-toms and Floor tom - 133 -  
Radiation of Sound - 64 -  
Radio frequency technique- 124 -  
RAID 1 (Mirroring) - 543 -  
RAID 2 (Bit Striping with error-  
correction) - 543 -  
RAID 3 (Bit Striping with Parity) - 544 -  
RAID 4 (Striping with Fixed Parity)  
- 544 -  
RAID 5 (Striping with Striped Parity)  
- 544 -  
RAID - 543 -  
Random access - 538 -  
Raw PCM data - 547 -  
Raymond Scott and the history of the  
sequencer - 441 -  
RCA 44 - 107 -  
RCA 77D and DX - 110 -  
Reading a circuit diagram - 303 -  
Real-world valves - 207 -  
Recent developments of the  
FRANCINSTIEN circuit - 617 -  
Re-circulating wavetable approach - 437 -  
Recording an orchestra - 151 -  
Recording Console - 654 -  
Recording formats - analogue machines  
- 476 -  
Red Book - 548 -  
REDD.37 / REDD.51 signal flow - 676 -  
REDD.47 - 679 -  
Reels - 858 -  
Regional Codes - 551 -  
Regulation & rectifier forward-resistance  
- 246 -  
Relationships between film and television  
frame rates - 851 -  
Reservoir capacitor - 244 -  
Resistor colour-code - 308 -  
Resistors - 306 -  
Resonance in air-columns, strings and bars  
- 44 -  
Reverberation - 82 -  
Reverberation, modal frequencies and the  
small room - 85 -  
Reverse leakage, PIV and avalanche  
(zener) diodes - 242 -  
Ribbon - 94 -  
Ring Modulation - 391 -  
Ripple voltage - 244 -  
RMS values - 17 -  
Rock-music brass-section - 137 -  
RØDE NT1A - 126 -  
Roland COSM - 778 -  
Roland Jazz Chorus 120 (JC-120) - 762 -  
Roland RSS System & Thorn EMI  
Sensaura - 634 -  
Room equalisation - 817 -  
Room modes - 83 -  
Rotary Head Digital Multi-track Formats  
- 537 -  
Rotating heads - 534 -  
RS232 and RS422 - 515 -  
RS232 - 515 -  
RS422 - 516 -  
SACD and DVD-A - 552 -  
SACD - 552 -  
Safety - 284 -  
Safety - 769 -  
Sampling Theory and Conversion - 485 -  
Sampling - 431 -  
SAOL - 594 -  
SATA - 541 -  
Scale distortion - 73 -  
Scrambling and Synchronisation - 531 -  
SCSI - 542 -

# Index

---

- SDII (Sound Designer File Format) - 545 -  
Sealed-Box - 785 -  
Semiconductor amplifiers - 710 -  
Semiconductors - 238 -  
Semi-pro audio levels - 320 -  
Sensitivity - 105 -  
Sequencer Programs - 451 -  
Sequencer Recording - 452 -  
Sequential Logic and State-Machines - 512 -  
Serial Digital Interface (SDI) - 837 -  
Serialism - 59 -  
Series and Parallel - 9 -  
Set-up and hold time - 513 -  
Shuffler and Spreader - 678 -  
Side drum (snare)- 133 -  
Signal generator - 297 -  
Signals and clocks - 513 -  
Signals in the time-domain and the frequency-domain - 43 -  
Signals - 344 -  
Signetics NE5534 and 5532 (dual) - 270 -  
Simple electric circuit - 7 -  
Sinc response - 558 -  
Sine wave oscillators - 331 -  
Sine waves are not music? - 314 -  
Sines and slews - 266 -  
Singing Arc - 321 -  
Slots - 796 -  
SM57 - 114 -  
SM58 - 113 -  
Small signal valves - 211 -  
Smoothing - 245 -  
SMPTE Drop-Frame Timecode - 854 -  
Software instruments - 579 -  
Software tools - 301 -  
Software tools - 567 -  
Soldering iron - 290 -  
Solid-state recorder - 553 -  
Solid-state rectifier and the power supply - 243 -  
Solving differential equations - 162 -  
Sound Intensity Level (SIL) - 60 -  
Sound Mixer Architecture and Circuit  
Blocks - 650 -  
Source music and underscore - 857 -  
Space charge - 186 -  
Spaced Omnis (A - B) technique - 141 -  
Spatial Hearing - 599 -  
Spatial Hearing - 81 -  
Spatial sound - 599 -  
SPDIF or IEC985 Type 2 Interface - 528 -  
Speed Stability - 476 -  
Spotting, Cues and Hits - 857 -  
Spreadsheet - 302 -  
Spring reverb - 376 -  
SRAM - 520 -  
Stability and compensation - 278 -  
Standard Levels and Level Meters - 642 -  
Standard Operating Levels and Line-up  
Tones - 649 -  
STC 4038 - 110 -  
STEED - 376 -  
Stereo microphone techniques - 140 -  
Stereo - 468 -  
Stereophony in large halls - 612 -  
String quartet - 135 -  
Strings instruments - 133 -  
Structured Audio - 593 -  
Sub-Woofer and the Band-Pass Enclosure - 807 -  
Sub-woofers for sound reinforcement - 808 -  
Superheterodyning instruments - 324 -  
Supro S6616 - 764 -  
Sweet spot - 612 -  
Switched-mode power-supplies - 736 -  
Switch-On "Thumps" - 718 -  
Synchronisation of Music to Picture - 856 -  
System Architecture - 650 -  
System Messages - 449 -  
Table of useful physical constants - 320 -  
Talkback - 657 -  
Talk-box Guitar Effect - 411 -  
Tape "Special Effects" - Musique  
Concrete - 483 -  
Tape Looping - 482 -  
Tape Speed - 476 -  
Telefunken and EMI REDD consoles - 672 -  
Teletronix LA-2a - 404 -  
Television signal - 825 -  
Telharmonium - 322 -  
Temporal masking - 76 -  
Test equipment - 291 -  
Tests - 775 -  
Text-to-Speech - 594 -  
TG12345 - 687 -  
The "Analogue" Interface - 435 -  
The "sound" of valves - 741 -  
Theoretical derivation of the masking curve - 75 -  
Theory of Harmony - 56 -  
Theory - 486 -  
Theremin - 324 -  
Thermal Effects - 797 -  
Thermal noise in triodes - 199 -  
Thermal Stability and Transistor Output  
Stage Protection - 714 -  
Thermal Stability - 715 -  
Thermionic emission and the diode valve - 185 -  
Timecode - 668 -  
Timecode - 853 -  
TL07x family - 269 -

# Index

---

- Tone-arm tracking - 463 -  
Too many channels - 627 -  
Tools of the trade - 290 -  
TOSlink optical Interface (now IEC 60958)  
Type II Optical or optical SPDIF - 530 -  
Track Structure - 550 -  
Transfer functions - 170 -  
Transformers - 14 -  
Transforming the low-pass filter to other  
types - 183 -  
Transients - 40 -  
Transition to digital video - 833 -  
Transmission lines - or, when is a wire not  
a wire? - 25 -  
Transmission of AES3 Formatted Data by  
Unbalanced Coaxial Cable- 530 -  
Trautonium and the invention of the  
relaxation oscillator - 328 -  
Treble Boosters - 384 -  
Treble-boost circuit - 366 -  
Treble-cut circuit - 363 -  
Tremolo - 381 -  
Trident - 697 -  
Triode or Pentode - 706 -  
Triode - 227 -  
Tri-state - 502 -  
Triumph of electromagnetism! - 341 -  
TTL Logic - 503 -  
Two Different Philosophies - 739 -  
Two-Loudspeaker Stereophony - 601 -  
Types of digital memory - 520 -  
Tyranny of the "Center" - 626 -  
U67 - 118 -  
U87 - 119 -  
Ultra Linear and Cathode-coupled  
Amplifiers - 707 -  
Ultrasoundics - 314 -  
Unbypassed Rk - 197 -  
Univox - 339 -  
USB as an audio interface - 532 -  
Useful reference information - 318 -  
User Bits - 855 -  
V72 Studioverstarker (Studio amplifier)  
- 682 -  
V77 Mikrofonverstarker (Microphone  
amplifier) - 684 -  
Valve Amplifiers - 701 -  
Valve envelopes - 211 -  
Valve output - transistor drive - 727 -  
Valve Parameters and design data - 196 -  
Vampower - 761 -  
Vari-mu compressors: the Altec Lansing  
436 and the Fairchild 660 and 670 - 396 -  
Vertical Interval Timecode (VITC) - 854 -  
VF14(M) - the scarcest valve in the world!  
- 217 -  
VF14(M) valve and possible equivalents  
- 231 -  
VHDL - 523 -  
Video compression systems - 843 -  
Video Timing Reference Signals - 835 -  
Violin and viola - 134 -  
Virtuous solution - 664 -  
Vocals - 137 -  
Vocoder - 409 -  
Voicing and the importance of high-input  
impedance at the amplifier - 348 -  
Voltage Controlled Filter (VCF) - 422 -  
Voltage Controlled Oscillator (VCO)  
- 419 -  
Voltage regulation - 281 -  
Vox 7120 - 759 -  
Vox AC15 - 752 -  
Vox AC30 - 754 -  
Vox T60- 757 -  
Vox - 752 -  
VST, DirectX and AU - 578 -  
VU Meter - 643 -  
Wah-wah - 385 -  
WAV Files - 545 -  
Wave effects - 65 -  
Wave field synthesis (WFS) - Holographic  
stereophony - 610 -  
Waveguide filtering - 438 -  
Waveshape distortion synthesis - 439 -  
Wavetable Synthesis and other Proprietary  
Synthesis Algorithms - 434 -  
Weber's Law - 71 -  
Wein bridge based mid-EQ - 370 -  
Wein-bridge oscillator - 333 -  
Western Electric Type 212- 225 -  
What on earth is a root-Hertz? - 274 -  
What type of capacitor should I use?  
- 303 -  
Wideband masking - 75 -  
Wind ensemble - 136 -  
WMA - 546 -  
Woodwind instruments - 135 -  
World of frequency - 41 -  
Wow and rumble - 462 -  
Wrappers - 578 -  
Yamaha NS-10 - 816 -  
Yellow Book - 548 -  
You can hear what you can't hear? - 314 -  
Zobel network - 722 -  
Z-Transform - 565 -